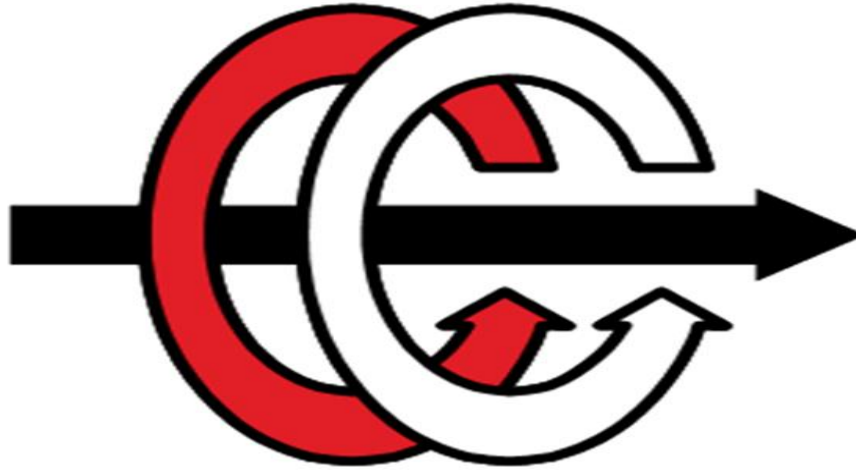


# EE464 - Software Project 1

## Ćuk Converter and Full-Bridge DC/DC Converter

---

### Report



#### Team Members:

*Cem Akıncı - 2093193*

*Ekin Alp Biçer - 2030385*

## INTRODUCTION

In this report, we are examining a Cuk converter that converts 9 V DC to -12 V DC. On question a, we analyzed the requirements and created a converter to fit the requirements. On second question, we compared input current of our converter to a similar sized buck-boost converter. On part c, we calculated the expected ripples of our system and compared it to the simulation results. On part d, we designed a controller that fixes the output to -12 V when the input varies between 9 – 11 V with 300 Hz. On last part, we have tested our controller when the input is an abrupt step from 9 V to 11 V.

## QUESTIONS

Q1)

a)

The requirements of our Cuk converter are given as :

- $V_d : 9 \text{ V}$
- $V_o : -12 \text{ V}$
- $I_o : 3 \text{ A}$
- $F_s : 100 \text{ kHz}$
- $\Delta V_o : 2\%$

Circuit schematic of our design is given illustrated in Figure 1.

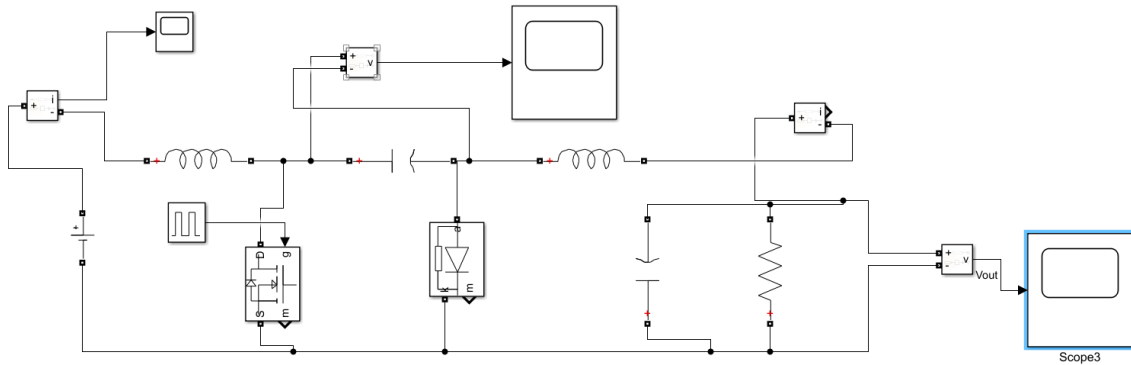


Figure 1 – Circuit schematic of the Cuk converter in Simulink.

$$V_o = \frac{D}{(1 - D)} V_d \quad [1]$$

Using Eq. 1 ,  $D = 0.571$ .

$$C_1 = \frac{D}{Rf_s \Delta V_{C1}/V_o} \quad [2]$$

Then by assuming that the maximum output voltage ripple is equal to the maximum voltage ripple of the C1 capacitor, the equation given in [2] is derived from the output current relation. Hence, it yields to  $C_1 = 71.37 \mu\text{F}$ .

$$C_2 = \frac{I_d}{2\omega_L \Delta V_o} \quad [3]$$

The value of the C2 capacitor is given in the Eq. 3. When the parameters are put in the given equation,  $C_2 = 10 \mu\text{F}$ . Steady State Output voltage ripple can be observed from below.

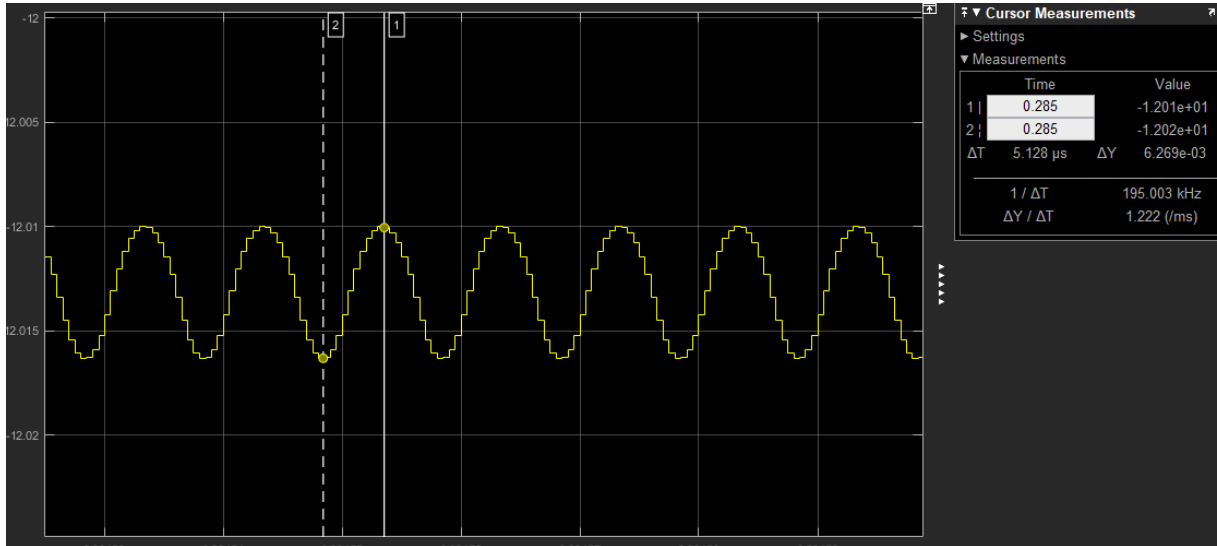


Figure 2 – Steady state output voltage ripple.

For the inductor selection, we assumed  $L_1 = L_2 = 1 \text{ mH}$ . However, we need to verify the selected values from the simulation results to see if they are consistent or not.

$$L_1 = \frac{DV_I}{f_s \Delta I_{Li}} \quad [4]$$

$$L_2 = \frac{(1 - D)V_o}{f_s \Delta I_{Lo}} \quad [5]$$

As the  $L_1$  and  $L_2$  values are chosen equal, the  $\Delta I_o = \Delta I_i$  and calculated as to be 0.051.

In the simulation results,  $\Delta I_i = 0.04701$  and  $\Delta I_o = 0.00158$  as illustrated in Figure 2 and Figure 3.

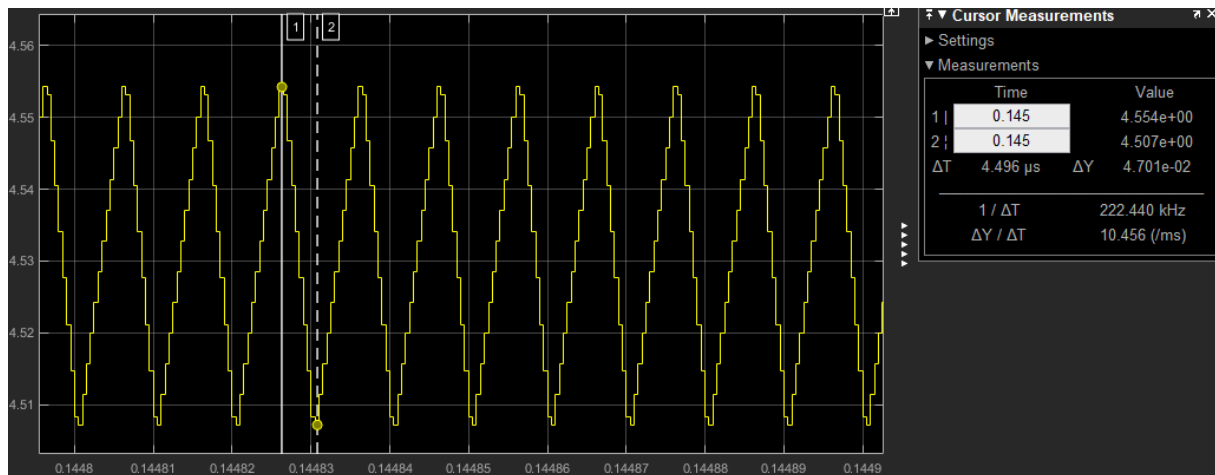


Figure 3 – Steady state input current ripple.


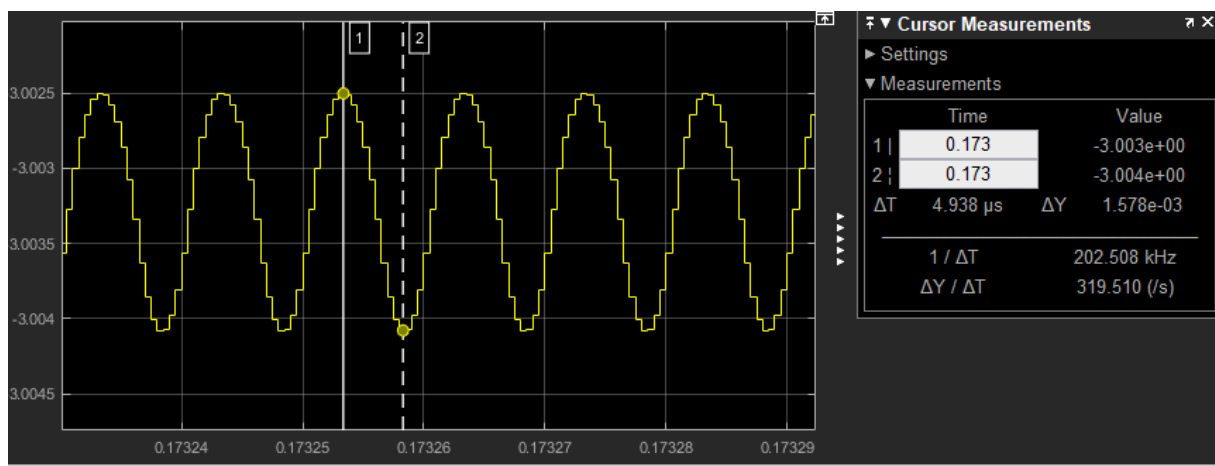


Figure 4 – Steady state output current ripple.

All of the required specifications are satisfied in this design and it is shown in Figures 2,3,4,5.

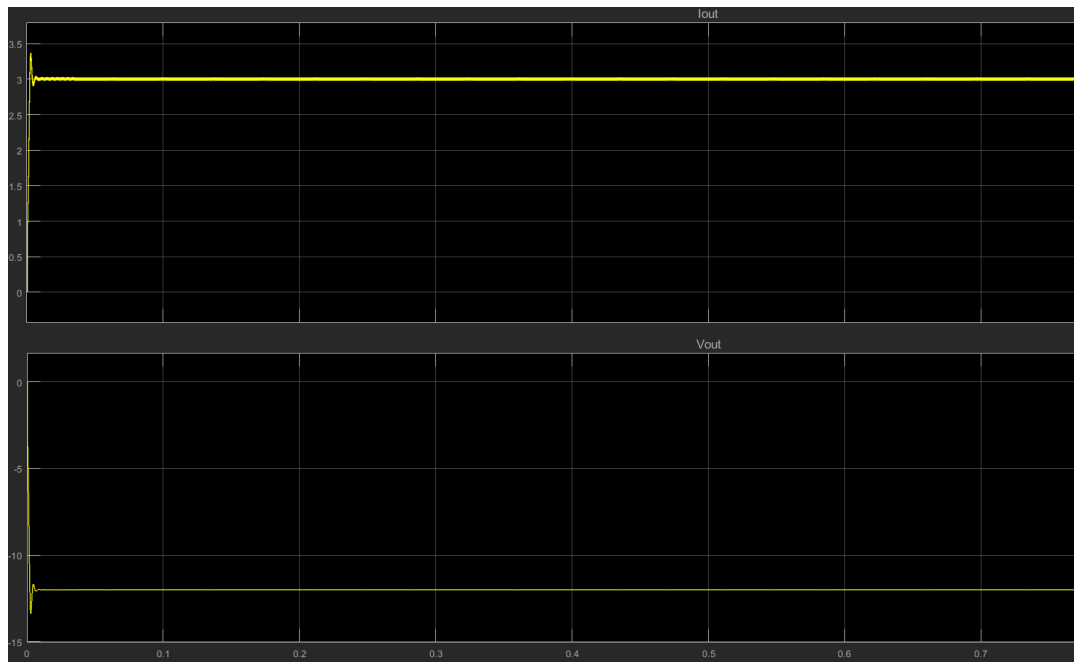

*Figure 5 – Output current and voltage waveforms at the steady state.*

We offer the following commercially available products for the components in our design:

**C1 Capacitor (72 uF)** : United Chemi-Con- EPAG451ELL720MM25S-ND

**Datasheet** : [http://www.chemi-con.co.jp/cgi-bin/CAT\\_DB/SEARCH/cat\\_db\\_al.cgi?e=e&j=p&pdfname=pag](http://www.chemi-con.co.jp/cgi-bin/CAT_DB/SEARCH/cat_db_al.cgi?e=e&j=p&pdfname=pag)

**C2 Capacitor (10 uF)** : Panasonic Electronic Components - ECA-1JM100I

**Datasheet** : <https://media.digikey.com/pdf/Data%20Sheets/Panasonic%20Electronic%20Components/ECA-xxM%20Series,TypeA.pdf>

**L1 and L2 inductors** : Würth Electronics - Inc.732-10759-2-ND

**Datasheet** : <https://katalog.we-online.de/pbs/datasheet/74404043102A.pdf>

**b)**

The input current waveform is plotted for the Ćuk converter and a similar sized buck-boost converter and the corresponding waveforms are illustrated in Figure 6-7-9.

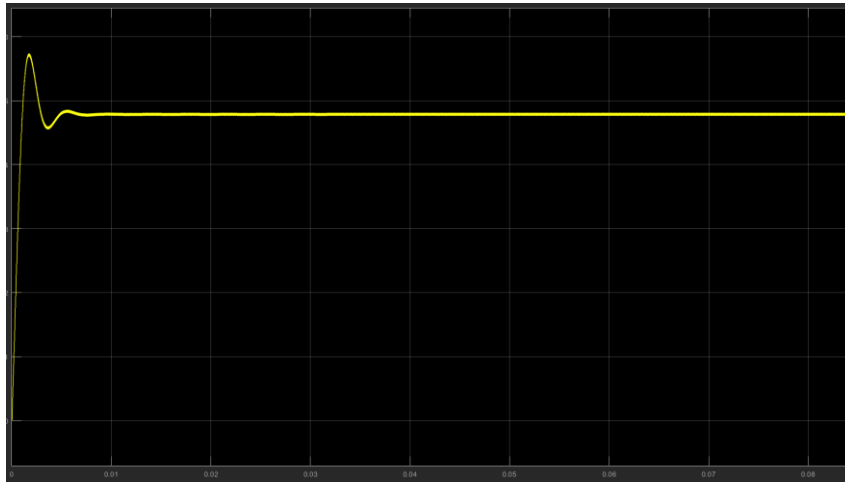


Figure 6 – Input current waveform of the Cuk converter.

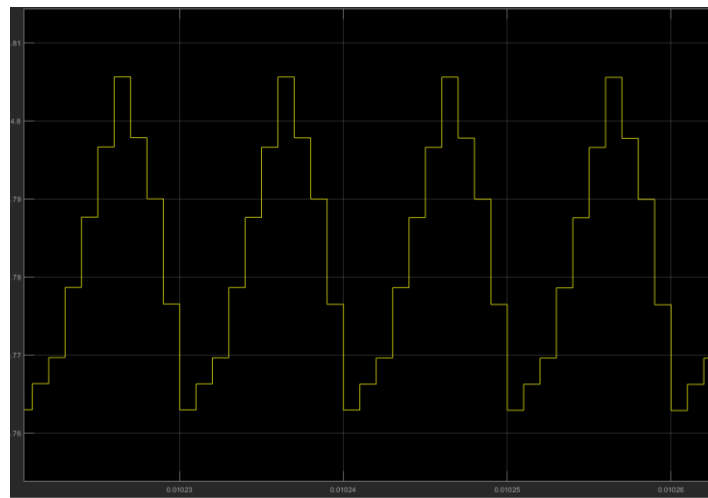


Figure 7 – Ripple of the input current waveform at the steady state.


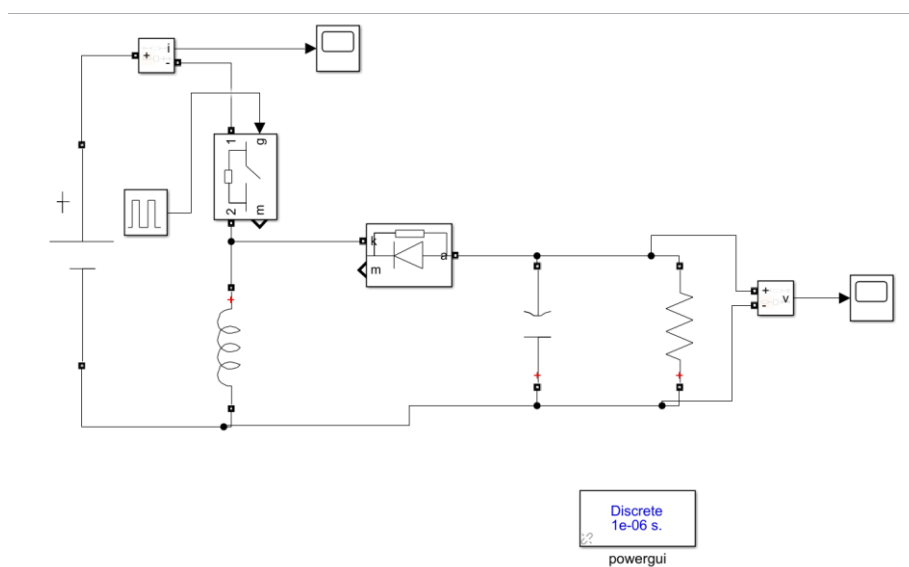


Figure 8 – Circuit schematic for the buck boost converter topology.

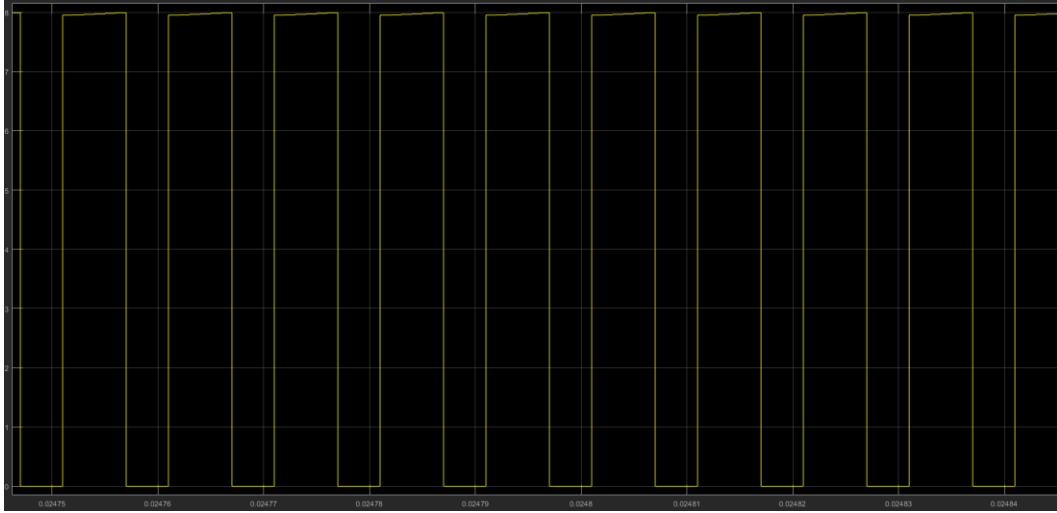

*Figure 9 – Input current waveform of the buck boost converter.*

The input current waveform of the buck boost converter and the Ćuk converter shows very different behaviour. The main difference is that the buck boost converter has a pulsed input current as can be observed in the Figure 9. The input current of the buck boost converter is discontinuous due to the power switch which pulses from zero to  $I_L$  every cycle. However, such an input current requires filtering. The Ćuk converter has a continuous input current waveform, since the input current is not affected from the switching. In addition to that, in the Ćuk converter the input current is ripple free, since it is fed through the inductor. Hence, it requires lower filtering than the buck boost converter.

It can be deduced that, the Ćuk converter is more advantageous than the buck boost converter topology in terms of the input current.

c)

Assuming that the output current is constant, when we plug our capacitor, resistance, frequency values to equation [2], we see the expected output ripple as :

$$\Delta V_o = \frac{I_o * D}{f * C1} = \frac{3 * \frac{4}{7}}{100000 * 72 * 10^{-6}} = 0.23 V = 0.198 \%$$

However, when we look at the simulation results, we observe the output voltage ripple as  $6.27 * 10^{-3}$  volts, which is much lower than what we expected.

Assuming  $V_o$  to be constant, when we plug our capacitor, resistance, frequency values to equation [5], we see the expected output ripple as :

$$\Delta I_o = \frac{V_{L2} * (1 - D)}{L2 * F} = \frac{12 * \left(1 - \frac{4}{7}\right)}{10^{-3} * 100000} = 0.051 A = 1.7 \%$$

However, when we inspect the simulation results, we observe the output current ripple as  $1.58 * 10^{-3}$  A, which is much lower than expected.

Since the simulation result is much lower than expected, we are content with the results. We believe that the reason behind this happy discrepancy is our assumptions. When we are

calculating the ripples, we assume constant voltage or constant current. Since they are also changing, this might have had an effect.

d)

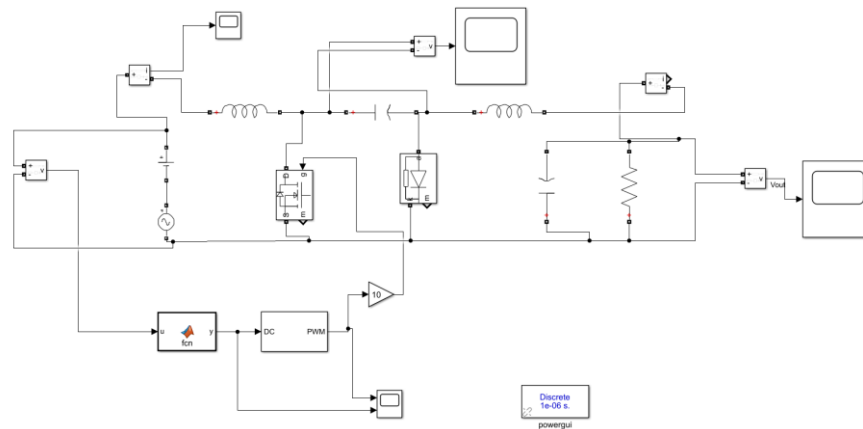


Figure 10 – Circuit schematic of the Ćuk converter with the controller which keeps the output voltage constant.

The controller is designed with a Matlab Function block in Simulink, which allows us to adjust the duty cycle as we wanted. The code written in the function block is as follows:

```
function y = fcn(u)

y = (12/(u+12))+0.05;
```

The duty cycle pin takes values between 0 and 1. We need a sinusoidal duty cycle which fluctuates between 0.54 and 0.6V in order to get a constant -12V output voltage with the changing input voltage. First, we used the formula above without the “+0.05”. However, the output voltage become -11V with this duty cycle. In order to fix the output voltage, 0.05 is added to the current duty cycle in order to get a fixed -12V output. Then, the gate of the MOSFET is driven with the generated PWM. The waveform of the DC and PWM is given in the Figure 11 and the output voltage waveform is illustrated in Figure 12.

Another important aspect for this to work is the c1 value. At first, we were having giant ripples at the output. When we checked the c1 voltage, we saw that it was not constant, indicating that the capacitor value is too small for the operation. After we increased c1 and c to 1 mF, the circuit started working like a charm.



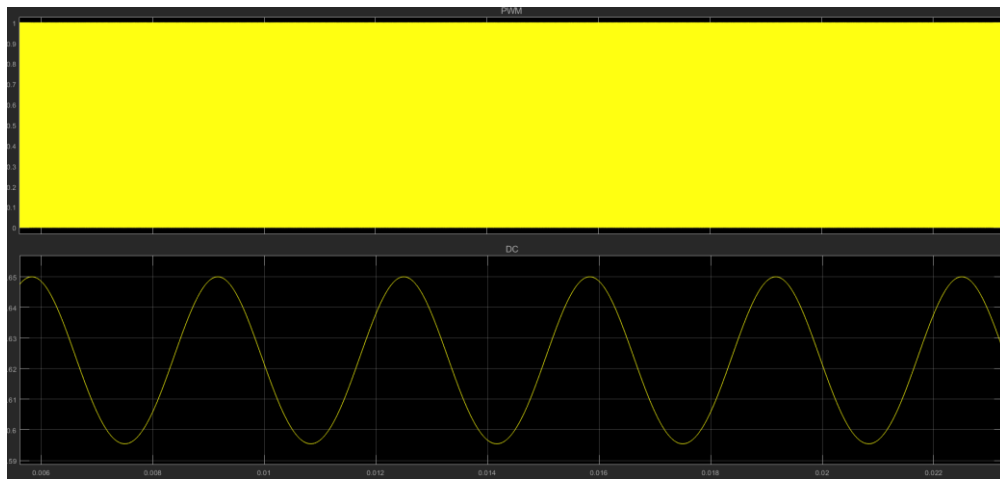


Figure 11 – Variation of the duty cycle and the generated pwm at the controller.



Figure 12 – Output voltage waveform of the circuit with the controller.

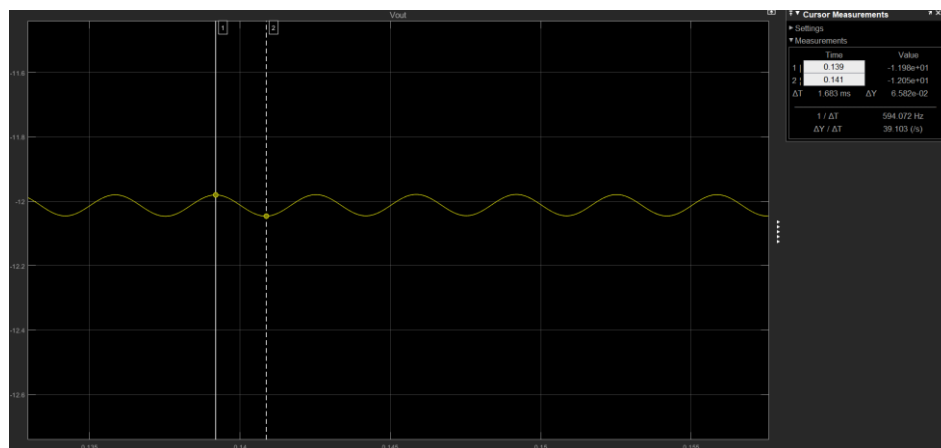


Figure 13 – Output voltage ripple waveform.

e)

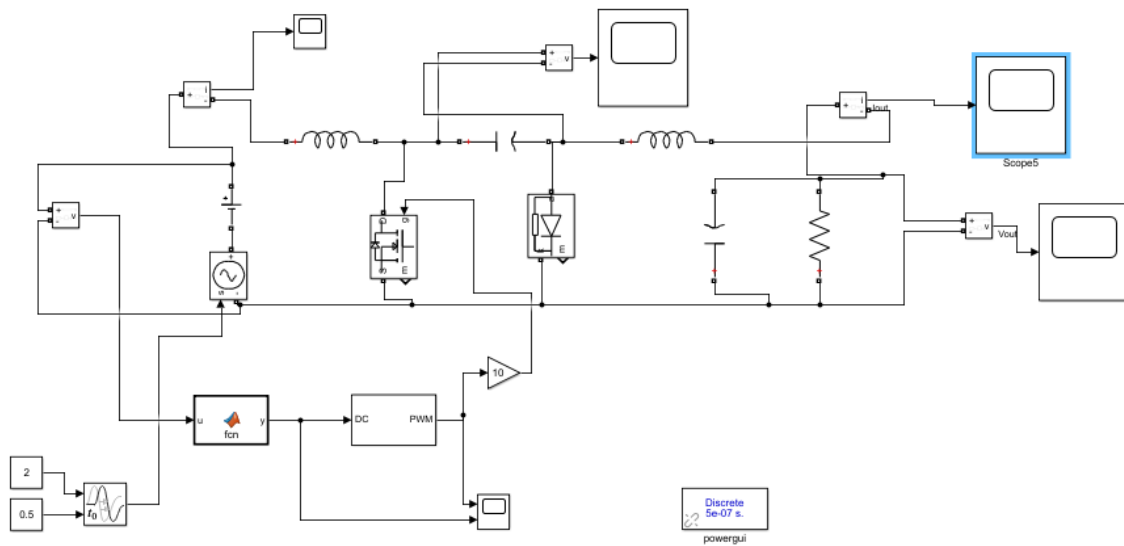


Figure 14 – The circuit with a step increase in input voltage.

On this part, we increased the input voltage as a step at 0.5 seconds. Since our controller is actually monitoring the input voltage, as the input voltage changes, we were expecting some transient oscillations, however, the output should not be affected. This was exactly the case. The controller works like a charm. After a few oscillations at  $t=0.5$ , the output voltage finally reached its desired value of -12V again.

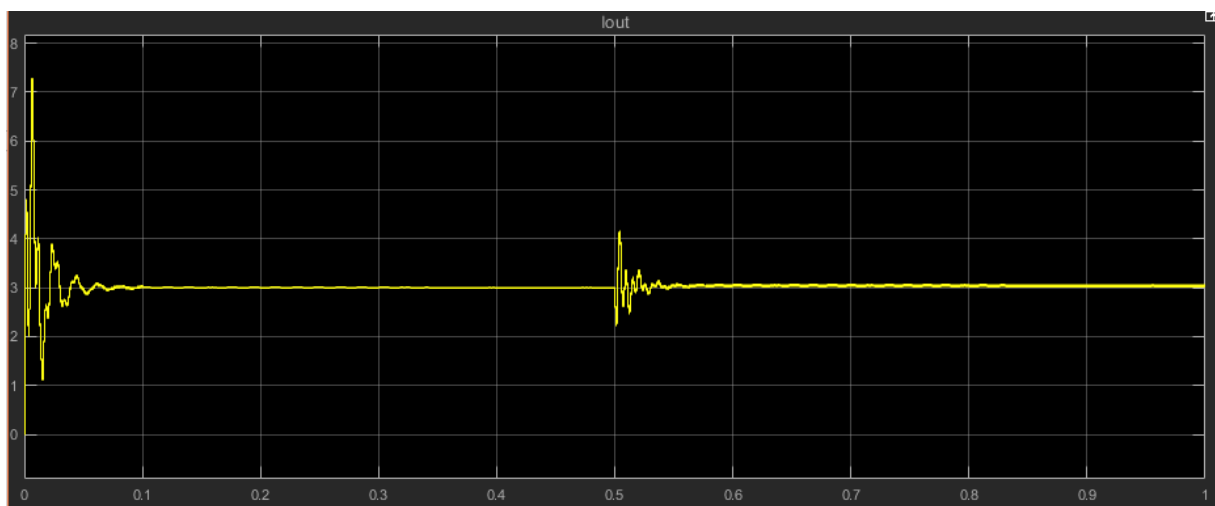


Figure 15 – Output current waveform during operation.

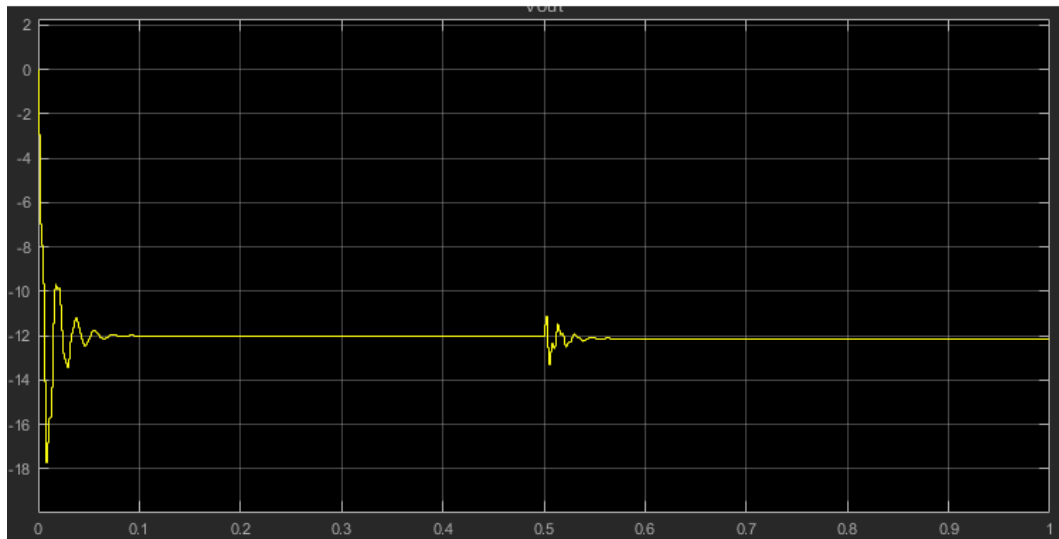


Figure 16 – Output voltage waveform during operation.

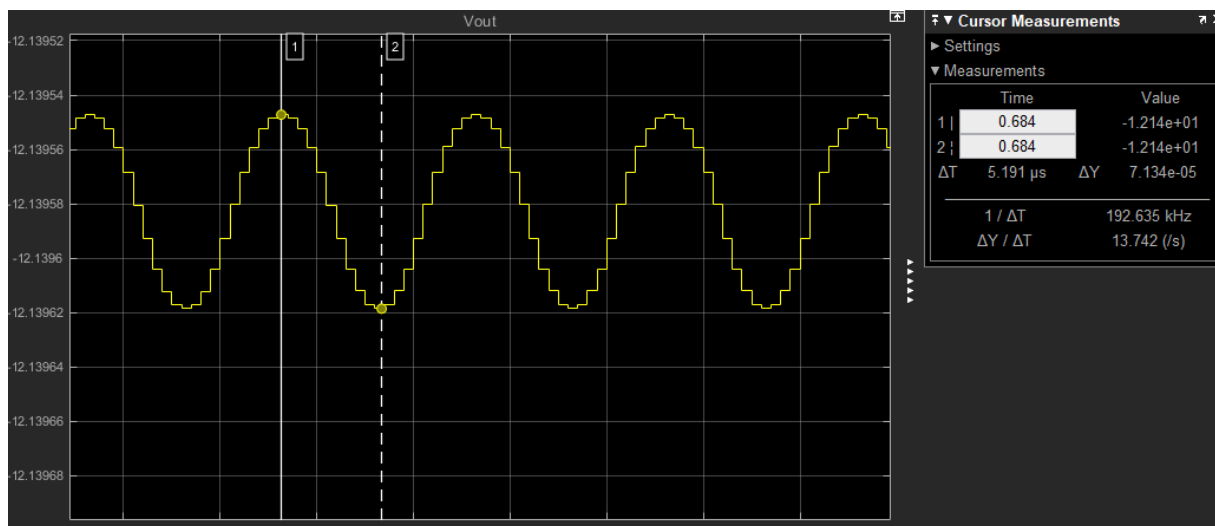


Figure 17 – Output voltage waveform during operation.

## CONCLUSION

In this simulation project, we learned how to design an inverting DC/DC converter, namely Cuk Converter. Based on the specifications, we tried to choose commercially available products to our design. After the design is completed, we observed the operation modes of the converter when the switch is ON and OFF and how it affects the ripples in the inductor current and the capacitor voltage. In addition to that, we analytically examined the circuit and compared our results with the simulation results. Everything except the ripple values were consistent with our expectations. The simulation is not ideal and the MOSFET's

internal parameters may have an effect on this result. We also examined the input current waveform of the Cuk converter and compared it with a similar sized buck boost converter's input current waveform. The difference between these two input waveforms results from the switching component's position in the converter circuit. In a buck boost converter, input current is pulsating because it is directly connected with the switch. However, in a Cuk converter, the input current is continuous. Finally, we designed a basic controller using the  $V_d$ ,  $V_o$ ,  $D$  relation in the Cuk converter and managed to keep the output voltage constant with changing input voltage.